

ASSIGNMENT 02

The questions for Assignment 2 are as follows

Please write the Assignment 2 very clearly.

- ✓ There is a processor GPIO that operates at 3.3V and sources or sinks 10mA.

Perform the following operations:

- a) Describe what is source or sink current.
- b) Find the GPIO drive strength of Arduino Nano, Uno, and ESP32S2.
- c) Draw a circuit with an explanation, to run a DC motor at 12V.
- d) Draw a circuit with an explanation to operate a relay at 5V.
- e) Perform the simulations in Easyeda.
- f) Draw the waveform and voltages at every node of your circuit.

Hint: Look at optocouplers, MOSFETs, and BJTs,.

You need to submit all the datasheets and explain how they are used.

The assignment should have the following topics.

- Table of contents, List of Tables.
 - Block diagrams.
 - Introduction.
 - Description.
 - EDA Schematic.
 - Simulation diagrams.
 - Datasheet references.
-
- ✓ Repeat the above with 5V 20mA GPIO.